

Practical 6

Aim: Write a VHDL Code to Implement 4- bit up-down counter using JK flip flop

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity U_D_Count_4b is
    Port ( M : in STD_LOGIC;
          Mb : inout STD_LOGIC;
          clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          cout : out STD_LOGIC_VECTOR (0 to 3));
end U_D_Count_4b;

architecture Behavioral of U_D_Count_4b is
    component JK_FF is
        Port ( clk : in STD_LOGIC;
              rst : in STD_LOGIC;
              J : in STD_LOGIC;
              K : in STD_LOGIC;
              Q : out STD_LOGIC;
              Qb : out STD_LOGIC);
    end component JK_FF;

    component and_gate is
        Port ( a : in STD_LOGIC;
              b : in STD_LOGIC;
              y : out STD_LOGIC);
    end component and_gate;

    component or_gate is
        Port ( a : in STD_LOGIC;
              b : in STD_LOGIC;
              y : out STD_LOGIC);
    end component or_gate;

    signal cout1:std_logic_vector(0 to 3);
    signal q1:std_logic_vector(0 to 3):="0000";
    signal d:std_logic_vector(0 to 2);
    signal u:std_logic_vector(0 to 2);
    signal c1:std_logic_vector(0 to 2);
    --signal Mb:std_logic;

begin
    Mb <= not M;
    z1:for i in 0 to 3 generate
```

```


f1: if (i=0) generate
  x1:JK_FF port map(clk,rst,'1','1',cout1(i),q1(i));


  end generate f1;

f2: if (i>0) generate
  x2:and_gate port map(cout1(i-1),Mb,d(i-1));
  x3:and_gate port map(q1(i-1),M,u(i-1));
  x4:or_gate port map(d(i-1),u(i-1),c1(i-1));
  x1:JK_FF port map(c1(i-1),rst,'1','1',cout1(i),q1(i));
  end generate f2;
end generate z1;
cout<=cout1;
end Behavioral;

```

RTL DIAGRAM:

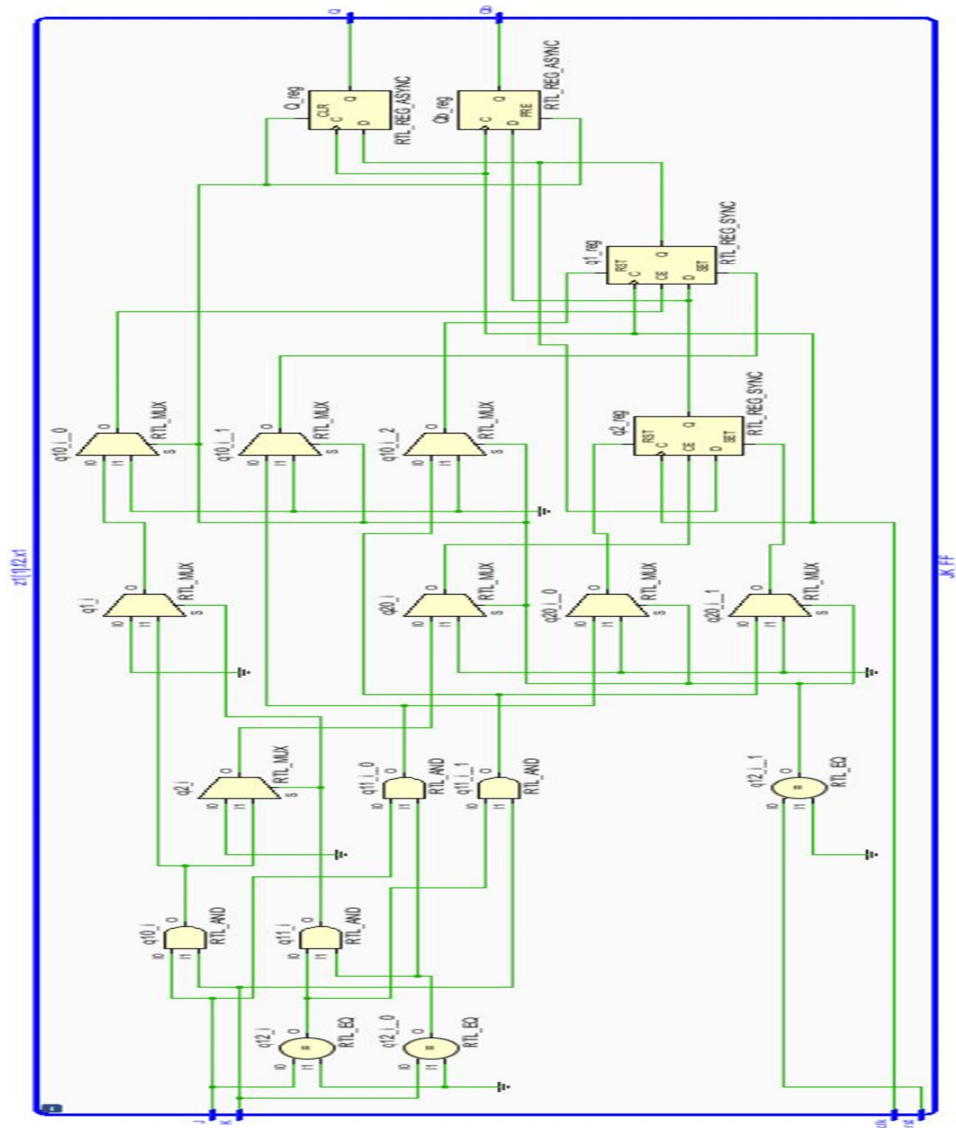

 

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_U_D_Count_4b is
-- Port ( );
end Tb_U_D_Count_4b;

architecture Behavioral of
Tb_U_D_Count_4b is
component U_D_Count_4b is
Port ( M : in STD_LOGIC;
Mb : inout STD_LOGIC;
clk : in STD_LOGIC;
rst : in STD_LOGIC;
cout : out
STD_LOGIC_VECTOR (0 to 3));
end component U_D_Count_4b;
signal m1,mb1,clk1,rst1:std_logic;
```

```
signal cout1:std_logic_vector(0 to
3);
```

```
begin
X1:U_D_Count_4b port
map(m1,mb1,clk1,rst1,cout1);
process
begin
rst1<='0';
wait for 5ns;
rst1<='1';
wait;
end process;
```

```
process
begin
clk1<='0';
```


```
wait for 5ns;
clk1<='1';
wait for 5ns;
end process;
```

```
process
begin
```

```
m1<='1';--upcount
wait for 500ns;
m1<='0';--downcount
wait;
end process;
```


```
end Behavioral;
```

SIMULATION WAVEFORM :

 

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	9	17600	0.05
FF	15	35200	0.04
IO	8	100	8.00

 

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	4	M	Mb	5.351	3.752	1.599	∞	input port clock
Path 2	∞	2	2	2	z1[1].f2.x1/Q_reg/C	cout[1]	4.116	3.316	0.800	∞	
Path 3	∞	2	2	2	z1[2].f2.x1/Q_reg/C	cout[2]	4.116	3.316	0.800	∞	
Path 4	∞	2	2	1	z1[3].f2.x1/Q_reg/C	cout[3]	4.116	3.316	0.800	∞	
Path 5	∞	2	2	2	z1[0].f1.x1/Q_reg/C	cout[0]	4.076	3.276	0.800	∞	
Path 6	∞	2	3	9	rst	z1[0].f1.x1/Q_reg/CLR	2.717	1.106	1.611	∞	input port clock
Path 7	∞	2	3	9	rst	z1[0].f1.x1/Qb_reg/PRE	2.717	1.106	1.611	∞	input port clock
Path 8	∞	2	3	9	rst	z1[1].f2.x1/Q_reg/CLR	2.717	1.106	1.611	∞	input port clock
Path 9	∞	2	3	9	rst	z1[1].f2.x1/Qb_reg/PRE	2.717	1.106	1.611	∞	input port clock
Path 10	∞	2	3	9	rst	z1[2].f2.x1/Q_reg/CLR	2.717	1.106	1.611	∞	input port clock

Maximum Combinational Delay: 5.351nSec

Aim: Write a VHDL Code to implement 4-bit serial in-parallel out shift register

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Sin_Pout_4b is
    Port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          I : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (0 to 3));
end Sin_Pout_4b;

architecture Behavioral of Sin_Pout_4b is
    component D_FF is
        Port ( clk : in STD_LOGIC;
              rst : in STD_LOGIC;
              D : in STD_LOGIC;
              Q : out STD_LOGIC;
              Qb : out STD_LOGIC);
    end component D_FF;
    signal u1:std_logic_vector(0 to 3);
    signal u2:std_logic_vector(0 to 3);
begin

    z1: for k in 0 to 3 generate
        f1:if(k=0) generate

            x1:D_FF port map(clk,rst,I,u1(k),u2(k));
        end generate f1;



        f2:if(k>0) generate

            x2:D_FF port map(clk,rst,u1(k-1),u1(k),u2(k));
        end generate f2;

    end generate z1;
    Q<=u1;

end Behavioral;
```

RTL DIAGRAM:

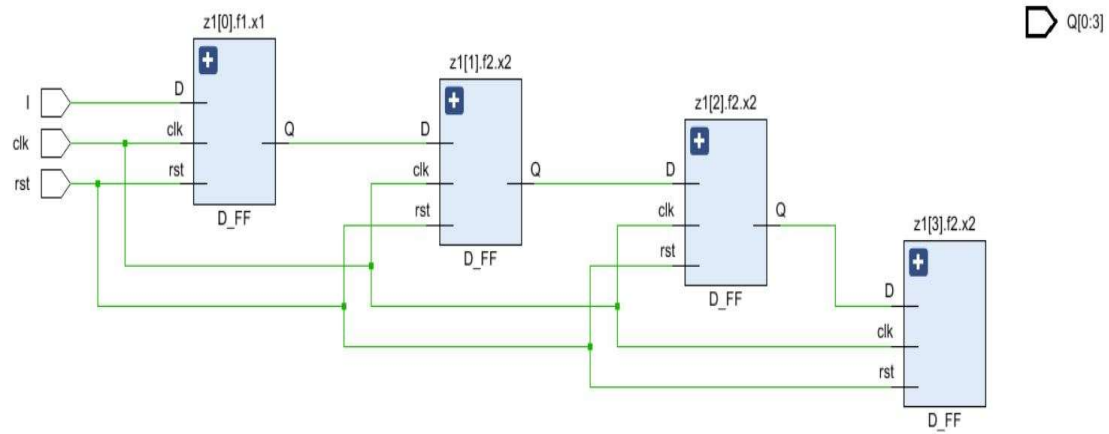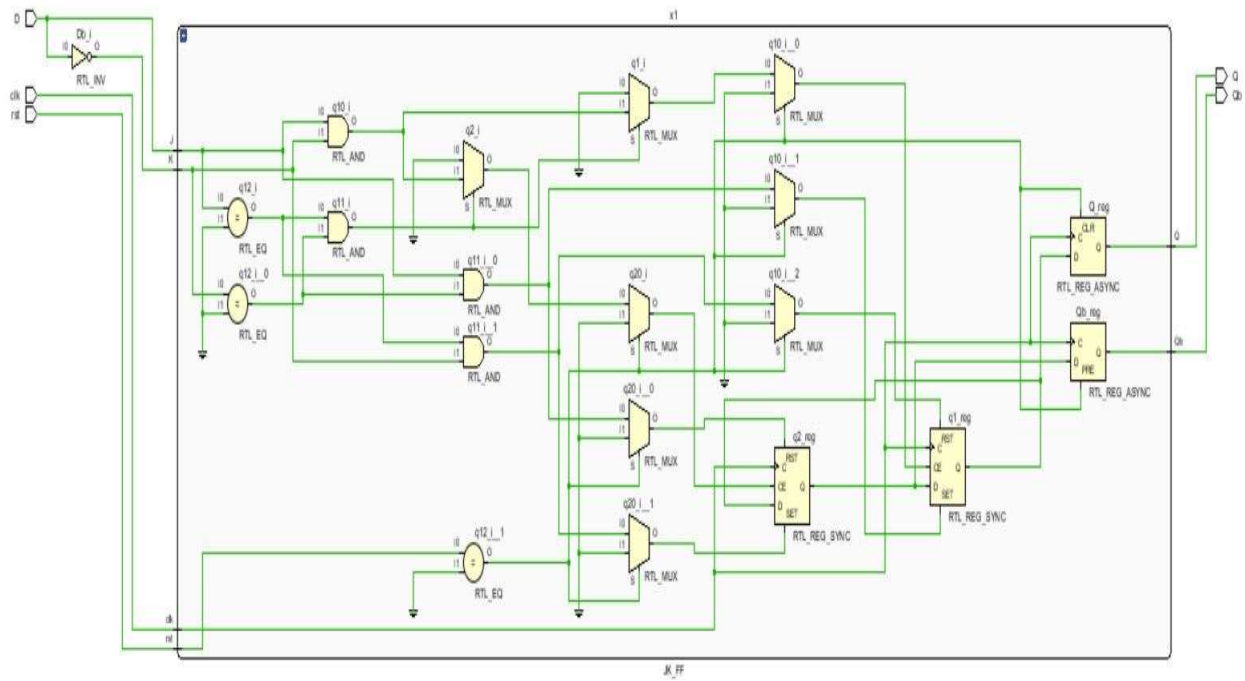

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_Sin_Pout_4b is
-- Port ( );
end Tb_Sin_Pout_4b;

architecture Behavioral of
Tb_Sin_Pout_4b is
component Sin_Pout_4b is
Port ( clk : in STD_LOGIC;
rst : in STD_LOGIC;
I : in STD_LOGIC;
Q : inout
STD_LOGIC_VECTOR (0 to 3));
end component Sin_Pout_4b;
signal k,clk1,rst1:std_logic;
signal Q1:std_logic_vector(0 to
3):="0000";

begin

X1:Sin_Pout_4b port
map(clk1,rst1,k,Q1);


process
begin
rst1<='0';
wait for 5ns;
rst1<='1';
wait;
end process;

process
begin
clk1<='0';
wait for 5ns;
clk1<='1';

wait for 5ns;
end process;


end Behavioral;
```

SIMULATION WAVEFORM :

 

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	5	17600	0.03
FF	8	35200	0.02
IO	7	100	7.00

 

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	2	z1[0].f1.x1/x1/Q_reg/C	Q[0]	4.076	3.276	0.800	∞	
Path 2	∞	2	2	2	z1[1].f2.x2/x1/Q_reg/C	Q[1]	4.076	3.276	0.800	∞	
Path 3	∞	2	2	2	z1[2].f2.x2/x1/Q_reg/C	Q[2]	4.076	3.276	0.800	∞	
Path 4	∞	2	2	1	z1[3].f2.x2/x1/Q_reg/C	Q[3]	4.076	3.276	0.800	∞	
Path 5	∞	2	3	5	rst	z1[0].f1.x1/x1/Q_reg/CLR	2.706	1.106	1.600	∞	input port clock
Path 6	∞	2	3	5	rst	z1[1].f2.x2/x1/Q_reg/CLR	2.706	1.106	1.600	∞	input port clock
Path 7	∞	2	3	5	rst	z1[2].f2.x2/x1/Q_reg/CLR	2.706	1.106	1.600	∞	input port clock
Path 8	∞	2	3	5	rst	z1[3].f2.x2/x1/Q_reg/CLR	2.706	1.106	1.600	∞	input port clock
Path 9	∞	2	3	1	l	z1[0].f1.x1/x1/q1_reg/D	1.906	1.106	0.800	∞	input port clock
Path 10	∞	2	3	5	rst	z1[1].f2.x2/x1/q1_reg/D	1.906	1.106	0.800	∞	input port clock

Maximum Combinational Delay: 4.076nSec

Aim: Write a VHDL Code to implement 4-bit ripple adder using generate statement

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity rpl_adder_4b is
    Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
          b : in STD_LOGIC_VECTOR (3 downto 0);
          c : in STD_LOGIC;
          s : out STD_LOGIC_VECTOR (3 downto 0);
          co : out STD_LOGIC);
end rpl_adder_4b;

architecture Behavioral of rpl_adder_4b is
    component fulladder is
        Port ( a : in STD_LOGIC;
              b : in STD_LOGIC;
              c : in STD_LOGIC;
              s : out STD_LOGIC;
              cout : out STD_LOGIC);
    end component fulladder;
    signal c1:std_logic_vector(0 to 2);
    begin
        z1: for i in 0 to 3 generate


            f1:if(i=0) generate
                x1:fulladder port map(a(i),b(i),c,s(i),c1(0));
            end generate f1;

            f2:if(i=3) generate
                x2:fulladder port map(a(i),b(i),c1(i-1),s(i),co);
            end generate f2;

            f3:if(0<i and i<3) generate
                x3:fulladder port map(a(i),b(i),c1(i-1),s(i),c1(i));
            end generate f3;

        end generate z1;
    end Behavioral;
```

RTL DIAGRAM:

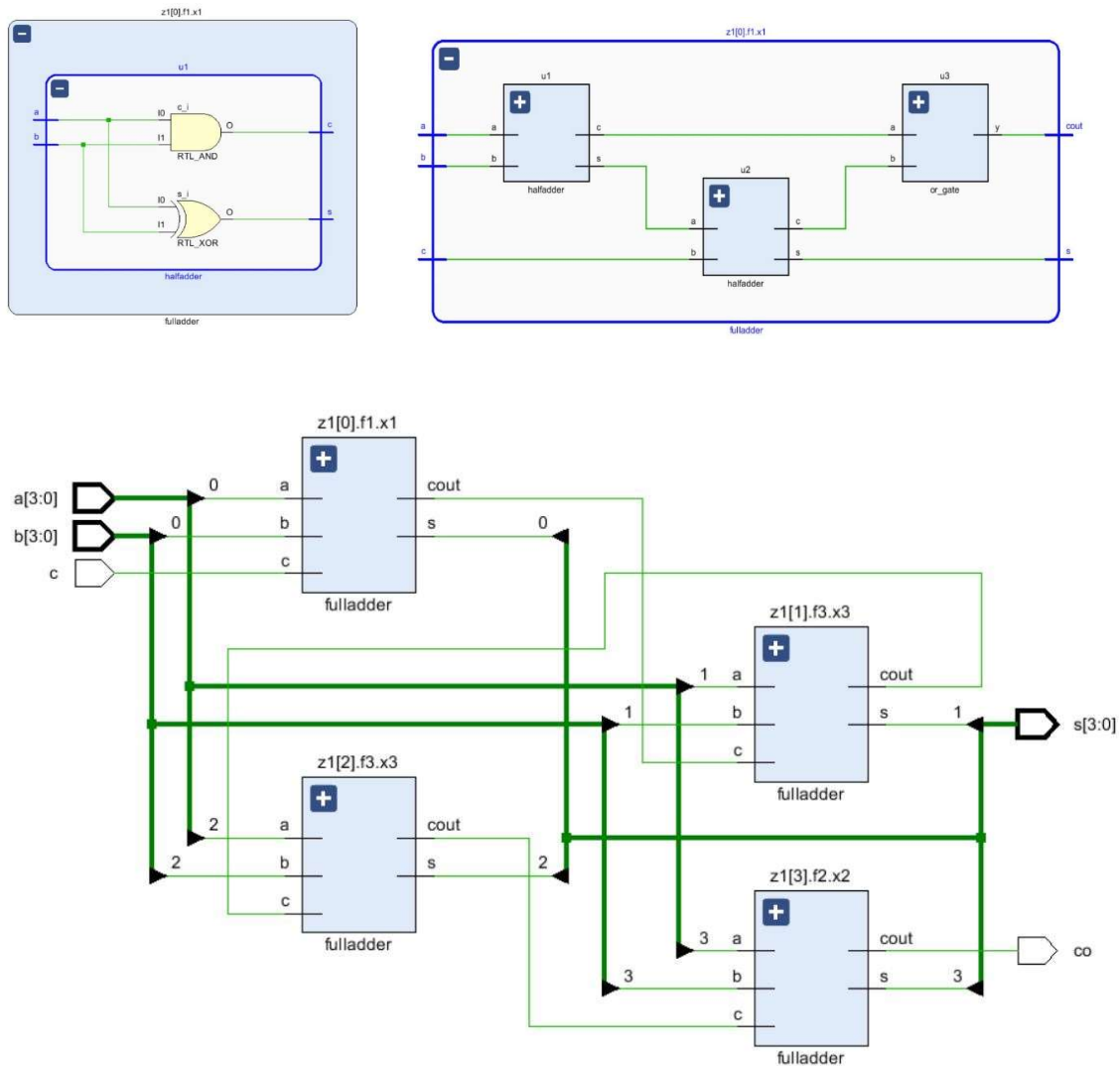

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_rpl_adder_4b is
-- Port ( );
end Tb_rpl_adder_4b;

architecture Behavioral of
Tb_rpl_adder_4b is
component rpl_adder_4b is
Port ( a : in STD_LOGIC_VECTOR
(3 downto 0);
b : in STD_LOGIC_VECTOR (3
downto 0);
```

```
c : in STD_LOGIC;
s : out STD_LOGIC_VECTOR
(3 downto 0);
co : out STD_LOGIC);
end component rpl_adder_4b;

signal a1 : STD_LOGIC_VECTOR (3
downto 0);
signal b1 : STD_LOGIC_VECTOR (3
downto 0);
signal c1 : STD_LOGIC;
signal s1 : STD_LOGIC_VECTOR (3
downto 0);
signal co1 : STD_LOGIC;
```

```
begin
X1:rpl_adder_4b port
map(a1,b1,c1,s1,co1);
process
begin
c1<='0';
a1<="0000";
b1<="0000";
wait for 10ns;

a1<="1111";
b1<="0000";
wait for 10ns;
```

a1<="1111";
b1<="1111";
wait for 10ns;

a1<="1111";
b1<="1010";
wait for 10ns;

c1<='1';

a1<="0000";
b1<="0000";
wait for 10ns;

a1<="1111";
b1<="0000";
wait for 10ns;

a1<="1111";

b1<="1111";
wait for 10ns;

a1<="1111";
b1<="1010";
wait for 10ns;
end process;

end Behavioral;

SIMULATION WAVEFORM :

The simulation waveform displays the following signals over time (0 ns to 80 ns):

- a1[3:0]**: 1111 (0-10 ns), 1111 (10-20 ns), 1111 (20-30 ns), 1111 (30-40 ns), 1111 (40-50 ns), 1111 (50-60 ns), 1111 (60-70 ns), 1111 (70-80 ns)
- b1[3:0]**: 1111 (0-10 ns), 1111 (10-20 ns), 1111 (20-30 ns), 1111 (30-40 ns), 1111 (40-50 ns), 1111 (50-60 ns), 1111 (60-70 ns), 1111 (70-80 ns)
- c1**: 1 (0-10 ns), 1 (10-20 ns), 1 (20-30 ns), 1 (30-40 ns), 1 (40-50 ns), 1 (50-60 ns), 1 (60-70 ns), 1 (70-80 ns)
- s1[3:0]**: 0000 (0-10 ns), 0000 (10-20 ns), 0000 (20-30 ns), 0000 (30-40 ns), 0000 (40-50 ns), 0000 (50-60 ns), 0000 (60-70 ns), 0000 (70-80 ns)
- c0[1]**: 1 (0-10 ns), 1 (10-20 ns), 1 (20-30 ns), 1 (30-40 ns), 1 (40-50 ns), 1 (50-60 ns), 1 (60-70 ns), 1 (70-80 ns)

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	4	17600	0.02
IO	14	100	14.00

Resource Utilization Summary:

- LUT: 1%
- IO: 14%

Name	Slack ^1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	4	5	3	a[1]	co	5.942	3.876	2.066	∞	input port clock
Path 2	∞	4	5	3	a[1]	s[2]	5.942	3.876	2.066	∞	input port clock
Path 3	∞	4	5	3	a[1]	s[3]	5.936	3.870	2.066	∞	input port clock
Path 4	∞	3	4	3	b[0]	s[1]	5.379	3.780	1.599	∞	input port clock
Path 5	∞	3	4	3	b[0]	s[0]	5.351	3.752	1.599	∞	input port clock

Maximum Combinational Delay: 5.942nSec