

Practical 5

Aim: Write a VHDL Code to implement JK Flipflop

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity JK_FF is
  Port ( clk : in STD_LOGIC;
        rst : in STD_LOGIC;
        J : in STD_LOGIC;
        K : in STD_LOGIC;
        Q : out STD_LOGIC;
        Qb : out STD_LOGIC);
end JK_FF;
```


```
architecture Behavioral of JK_FF is
  signal q1:std_logic:='0';
  signal q2:std_logic:='1';
```

```
begin

  process(rst,clk,J,K)
  begin
    if (rst='0') then
      Q<='0';
      Qb<='1';
    elsif(rising_edge(clk)) then
      if(J = '1' and K = '0')then
        q1<='1';
        q2<='0';
      elsif(J = '0' and K = '1') then
        q1<='0';
        q2<='1';
      elsif(J = '0' and K = '0') then
        q1<= q1;
        q2<=q2;
      elsif(J ='1' and K ='1') then
        q1<= q2;
        q2<= q1;
      end if;
      Q<=q1;
      Qb<=q2;
    end if;
  end process;

end Behavioral;
```

RTL DIAGRAM:

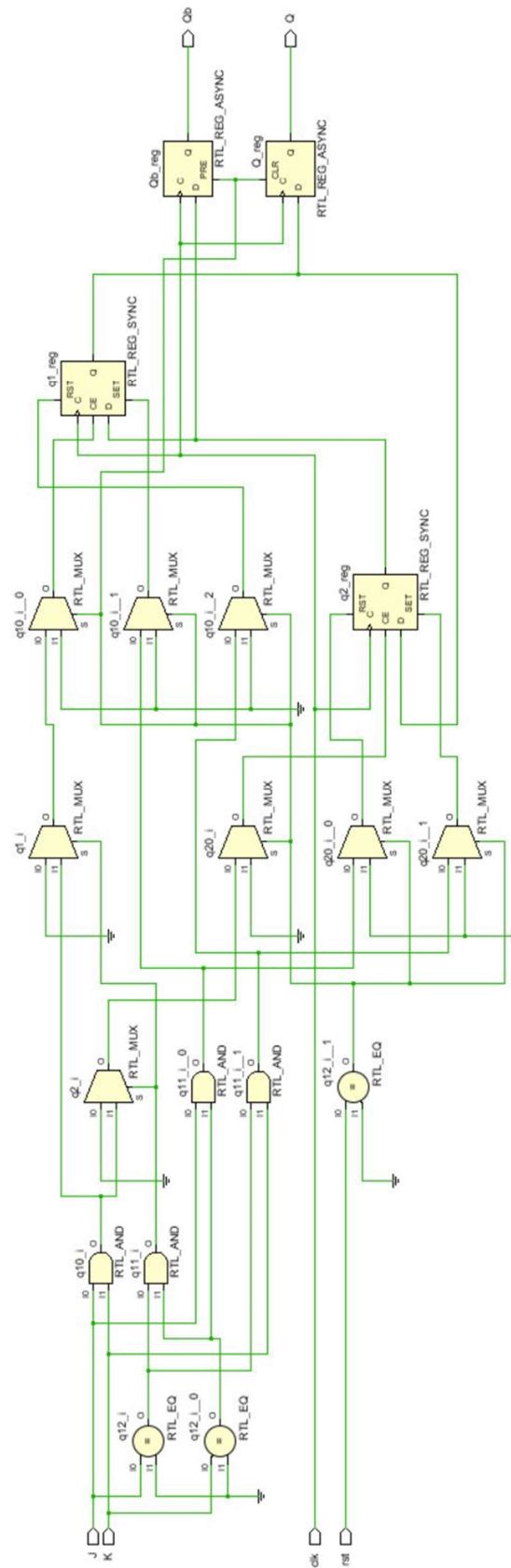

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_JK_FF is
-- Port ( );
end Tb_JK_FF;

architecture Behavioral of
Tb_JK_FF is

component JK_FF is
Port ( clk : in STD_LOGIC;
      rst : in STD_LOGIC;
      J : in STD_LOGIC;
      K : in STD_LOGIC;
      Q : out STD_LOGIC;
      Qb : out STD_LOGIC);
end component JK_FF;
signal clk,rst,J,K,Q,Qb:std_logic;

begin
x1:JK_FF port
map(clk,rst,J,K,Q,Qb);

process
begin
K<='0';
wait for 10ns;

J<='1';
K<='0';
wait for 10ns;

J<='0';
K<='1';
wait for 10ns;


J<='1';
K<='1';
wait for 10ns;

end process;

process
begin
rst<='0';
wait for 10ns;
rst<='1';
J<='0';


end Behavioral;
```

SIMULATION WAVEFORM :

 

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	2	17600	0.01
FF	4	35200	0.01
IO	6	100	6.00

 

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	1	Q_reg/C	Q	4.076	3.276	0.800	∞	
Path 2	∞	2	2	1	Qb_reg/C	Qb	4.076	3.276	0.800	∞	
Path 3	∞	2	3	3	rst	Q_reg/CLR	2.693	1.106	1.587	∞	input port clock
Path 4	∞	2	3	3	rst	Qb_reg/PRE	2.693	1.106	1.587	∞	input port clock
Path 5	∞	2	3	2	K	q1_reg/D	1.932	1.132	0.800	∞	input port clock
Path 6	∞	2	3	2	J	q2_reg/D	1.906	1.106	0.800	∞	input port clock
Path 7	∞	1	1	3	q1_reg/C	Q_reg/D	0.808	0.456	0.352	∞	
Path 8	∞	1	1	3	q2_reg/C	Qb_reg/D	0.808	0.456	0.352	∞	

Maximum Combinational Delay: 4.076nSec

Aim: Write a VHDL Code to implement D Flipflop

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity D_FF is
  Port ( clk : in STD_LOGIC;
        rst : in STD_LOGIC;
        D : in STD_LOGIC;
        Q : out STD_LOGIC;
        Qb : out STD_LOGIC);
end D_FF;

architecture Behavioral of D_FF is
  component JK_FF is
    Port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          J : in STD_LOGIC;
          K : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qb : out STD_LOGIC);
  end component JK_FF;
  signal Db:STD_LOGIC;

  begin
    Db<= not D;
    x1:JK_FF port map(clk,rst,D,Db,Q,Qb);

  end Behavioral;
```

RTL DIAGRAM:

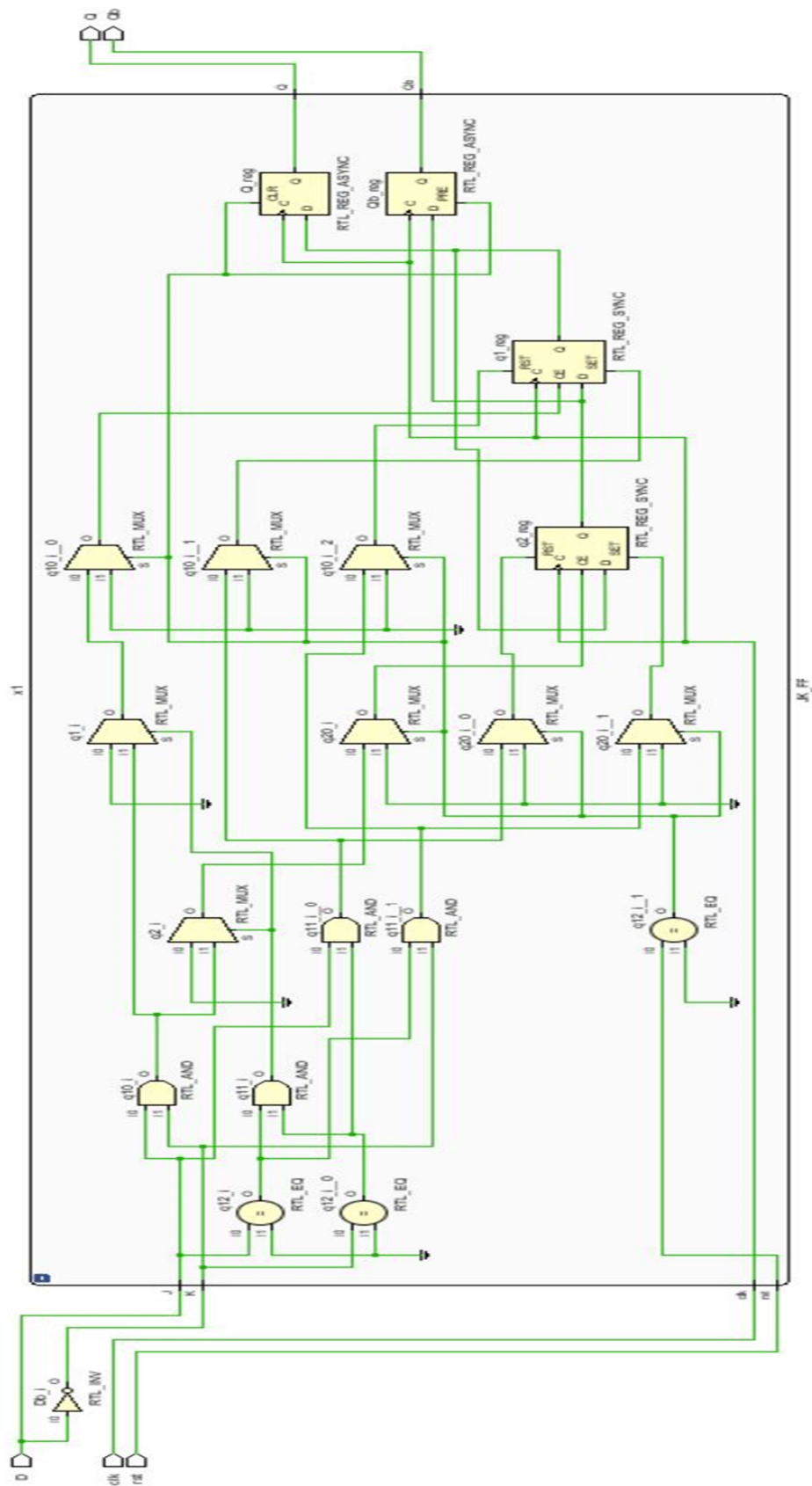

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity Tb_D_FF is
-- Port ( );
end Tb_D_FF;

architecture Behavioral of
Tb_D_FF is
component D_FF is
Port ( clk : in STD_LOGIC;
      rst : in STD_LOGIC;
      D : in STD_LOGIC;
      Q : out STD_LOGIC;
      Qb : out STD_LOGIC);
end component D_FF;

rst<='1';
wait for 50ns;
end process;
Process
begin
D<='0';
wait for 10ns;
D<='1';
wait for 10ns
end process;


end Behavioral;
```

SIMULATION WAVEFORM :

 

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	2	17600	0.01
FF	4	35200	0.01
IO	5	100	5.00

 

Name	Slack ^1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	1	x1/Q_reg/C	Q	4.076	3.276	0.800	∞	
Path 2	∞	2	2	1	x1/Qb_reg/C	Qb	4.076	3.276	0.800	∞	
Path 3	∞	2	3	3	rst	x1/Q_reg/CLR	2.693	1.106	1.587	∞	input port clock
Path 4	∞	2	3	3	rst	x1/Qb_reg/PRE	2.693	1.106	1.587	∞	input port clock
Path 5	∞	2	3	3	rst	x1/q1_reg/D	1.932	1.132	0.800	∞	input port clock
Path 6	∞	2	3	2	D	x1/q2_reg/D	1.906	1.106	0.800	∞	input port clock
Path 7	∞	1	1	2	x1/q1_reg/C	x1/Q_reg/D	0.801	0.456	0.345	∞	
Path 8	∞	1	1	2	x1/q2_reg/C	x1/Qb_reg/D	0.801	0.456	0.345	∞	

Maximum Combinational Delay: 4.076nSec