

## **Practical 7**

**Aim:** Write a VHDL Code to Implement 16 bit adder using behavioral modeling with generic

### **Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity adder_16b_bh is
generic(N : integer:=15);
  Port ( a : in STD_LOGIC_VECTOR (15 downto 0);
        b : in STD_LOGIC_VECTOR (15 downto 0);
        c : in STD_LOGIC;
        s : out STD_LOGIC_VECTOR (15 downto 0);
        co : out STD_LOGIC);
end adder_16b_bh;

architecture Behavioral of adder_16b_bh is

begin
process(a,b,c)
variable i:integer:=0;
variable c1:std_logic_vector( N+1 downto 0);
begin
c1(0):= c;
l1:for i in 0 to N loop

s(i)<=a(i) xor b(i) xor c1(i);
c1(i+1):= (a(i) and b(i)) or (b(i) and c1(i)) or (a(i) and c1(i));
end loop l1;
co<=c1(N+1);
end process;
end Behavioral;
```

## RTL DIAGRAM:

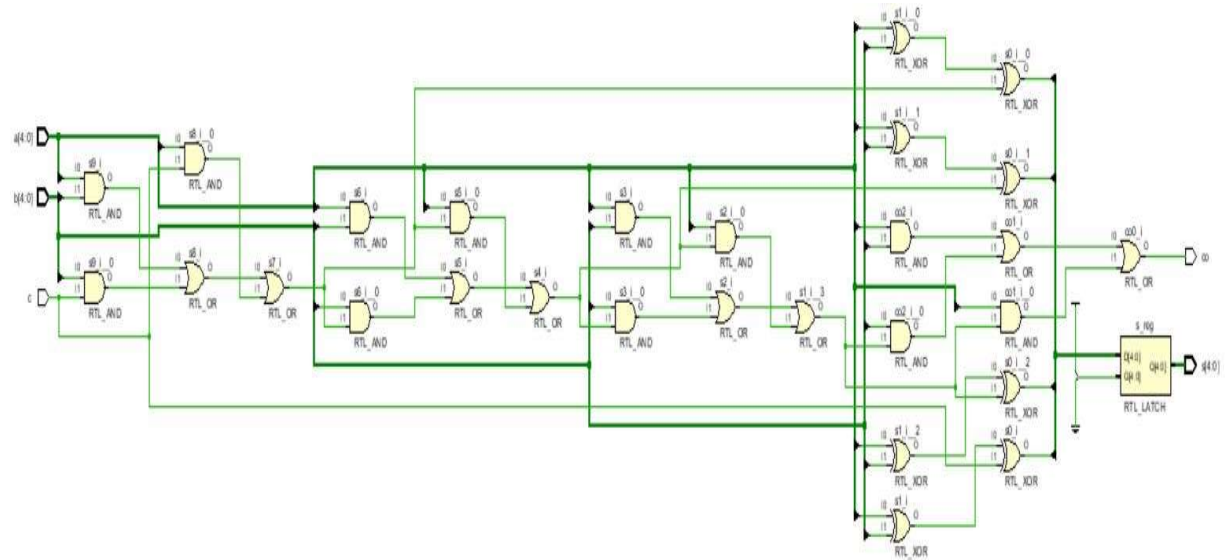

## Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_adder_16b_bh is
generic(N : integer:=15);
-- Port ( );
end Tb_adder_16b_bh;

architecture Behavioral of
Tb_adder_16b_bh is
component adder_16b_bh is
Port ( a : in
STD_LOGIC_VECTOR (N downto
0);
b : in STD_LOGIC_VECTOR
(N downto 0);
c : in STD_LOGIC;
s : out STD_LOGIC_VECTOR
(N downto 0);
co : out STD_LOGIC);
end component adder_16b_bh;

signal a1 : STD_LOGIC_VECTOR (N
downto 0);
```

```
signal b1 : STD_LOGIC_VECTOR (N
downto 0);
signal c1 : STD_LOGIC;
signal s1 : STD_LOGIC_VECTOR (N
downto 0);
signal c01 : STD_LOGIC;
begin
X1:adder_16b_bh port
map(a1,b1,c1,s1,c01);
process
begin
c1<='0';
a1<="0000000000000000";
b1<="0000000000000000";
wait for 10ns;

a1<="1111111111111111";
b1<="0000000000000000";
wait for 10ns;

a1<="1111111111111111";
b1<="1111111111111111";
wait for 10ns;
```

```
a1<="1111111111111111";
b1<="1010101010101010";
wait for 10ns;
```

```
c1<='1';
a1<="0000000000000000";
b1<="0000000000000000";
wait for 10ns;
```


```
a1<="1111111111111111";
b1<="0000000000000000";
wait for 10ns;
```

```
a1<="1111111111111111";
b1<="1111111111111111";
wait for 10ns;
```

```
a1<="1111111111111111";
b1<="1010101010101010";
wait for 10ns;
end process;
```


```
end Behavioral;
```

**SIMULATION WAVEFORM :**

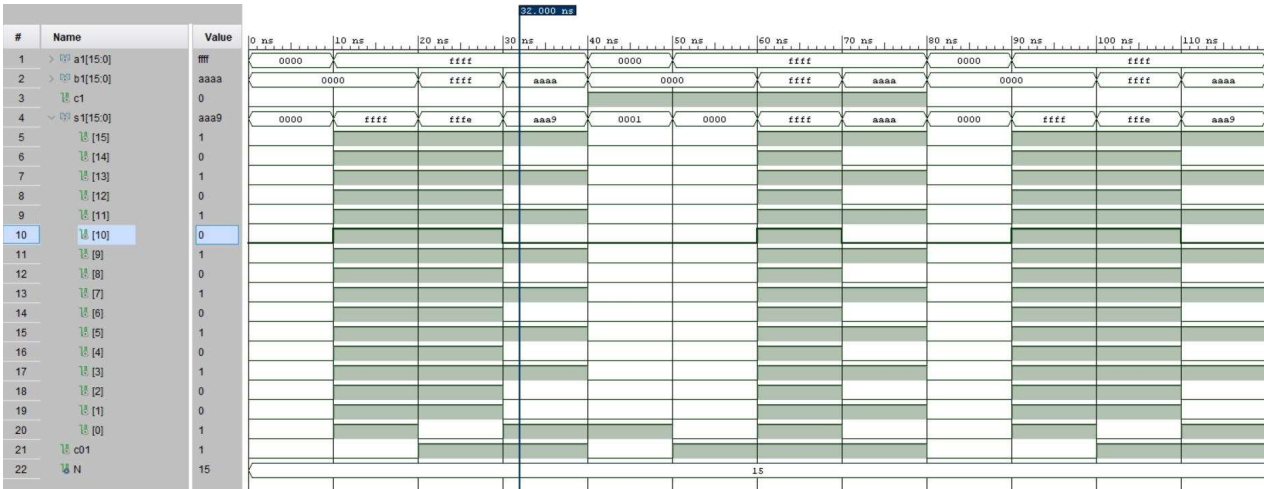

**SYNTHESIS SUMMARY:**

Resource	Utilization	Available	Utilization %
LUT	16	17600	0.09
IO	50	100	50.00

 

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	10	11	3	a[0]	co	9.480	4.612	4.868	∞	input port clock
Path 2	∞	10	11	3	a[0]	s[14]	9.480	4.612	4.868	∞	input port clock
Path 3	∞	10	11	3	a[0]	s[15]	9.474	4.606	4.868	∞	input port clock
Path 4	∞	9	10	3	a[0]	s[12]	8.895	4.494	4.401	∞	input port clock
Path 5	∞	9	10	3	a[0]	s[13]	8.895	4.494	4.401	∞	input port clock
Path 6	∞	8	9	3	a[0]	s[10]	8.310	4.376	3.934	∞	input port clock
Path 7	∞	8	9	3	a[0]	s[11]	8.310	4.376	3.934	∞	input port clock
Path 8	∞	7	8	3	a[0]	s[8]	7.725	4.258	3.467	∞	input port clock
Path 9	∞	7	8	3	a[0]	s[9]	7.725	4.258	3.467	∞	input port clock
Path 10	∞	6	7	3	a[0]	s[6]	7.140	4.140	3.000	∞	input port clock

Maximum Combinational Delay: 9.480nSec