

## Practical 2

**Aim:** Write a VHDL code to implement 3x8 decoder using behavioral modelling

### Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity Decoder\_3x8 is

```
Port ( i : in STD_LOGIC_VECTOR (2 downto 0);
      y : out STD_LOGIC_VECTOR (7 downto 0) );
end Decoder_3x8;
```


architecture Behavioral of Decoder\_3x8 is

```
begin
process(i)
begin
```

case(i) is

```
when "000" => y<="00000001";
when "001" => y<="00000010";
when "010" => y<="00000100";
when "011" => y<="00001000";
when "100" => y<="00010000";
when "101" => y<="00100000";
when "110" => y<="01000000";
when "111" => y<="10000000";
when others => y<="10000000";
end case;
end process;
end Behavioral;
```

### RTL DIAGRAM:

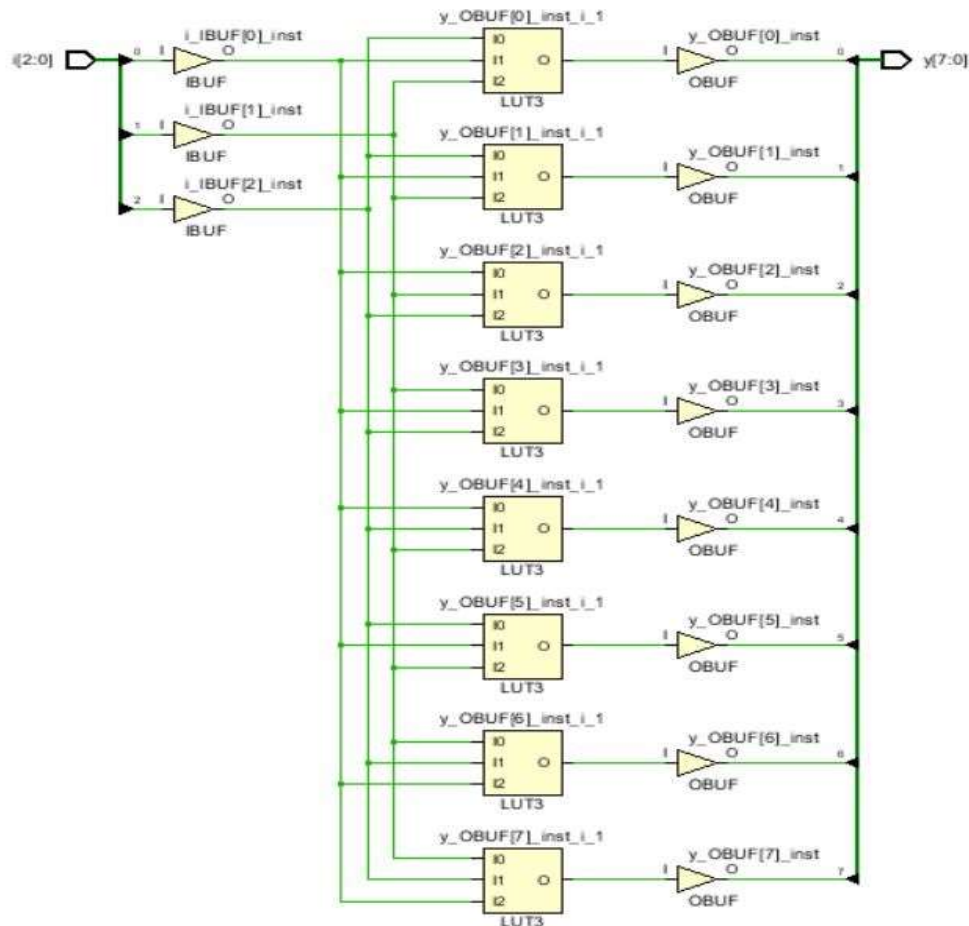

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_Decoder_3x8 is
-- Port ( );
end Tb_Decoder_3x8;

architecture Behavioral of Tb_Decoder_3x8
is
component Decoder_3x8 is
Port ( i : in STD_LOGIC_VECTOR (2 downto
0);
y : out STD_LOGIC_VECTOR (7 downto 0));
end component Decoder_3x8;
signal i:std_logic_vector(2 downto 0);
signal y:std_logic_vector(7 downto 0);

begin
x1:Decoder_3x8 port map(i,y);
process
begin
i <="000";
wait for 10ns;

i <="001";
wait for 10ns;

i <="010";
wait for 10ns;

i <="011";
wait for 10ns;

i <="100";
wait for 10ns;

i <="101";
wait for 10ns;

i <="110";
wait for 10ns;

i <="111";
wait;
end process;
wait for 10ns;
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tb_Decoder_3x8 is
-- Port ( );
end Tb_Decoder_3x8;

architecture Behavioral of Tb_Decoder_3x8
is
component Decoder_3x8 is
Port ( i : in STD_LOGIC_VECTOR (2 downto
0);
y : out STD_LOGIC_VECTOR (7 downto 0));
end component Decoder_3x8;
signal i:std_logic_vector(2 downto 0);
signal y:std_logic_vector(7 downto 0);

begin
x1:Decoder_3x8 port map(i,y);
process
begin
i <="000";
wait for 10ns;

i <="001";
wait for 10ns;

i <="010";
wait for 10ns;

i <="011";
wait for 10ns;

i <="100";
wait for 10ns;


i <="101";
wait for 10ns;

i <="110";
wait for 10ns;

i <="111";
wait;
end process;
wait for 10ns;
end Behavioral;

```

**SIMULATION WAVEFORM :**

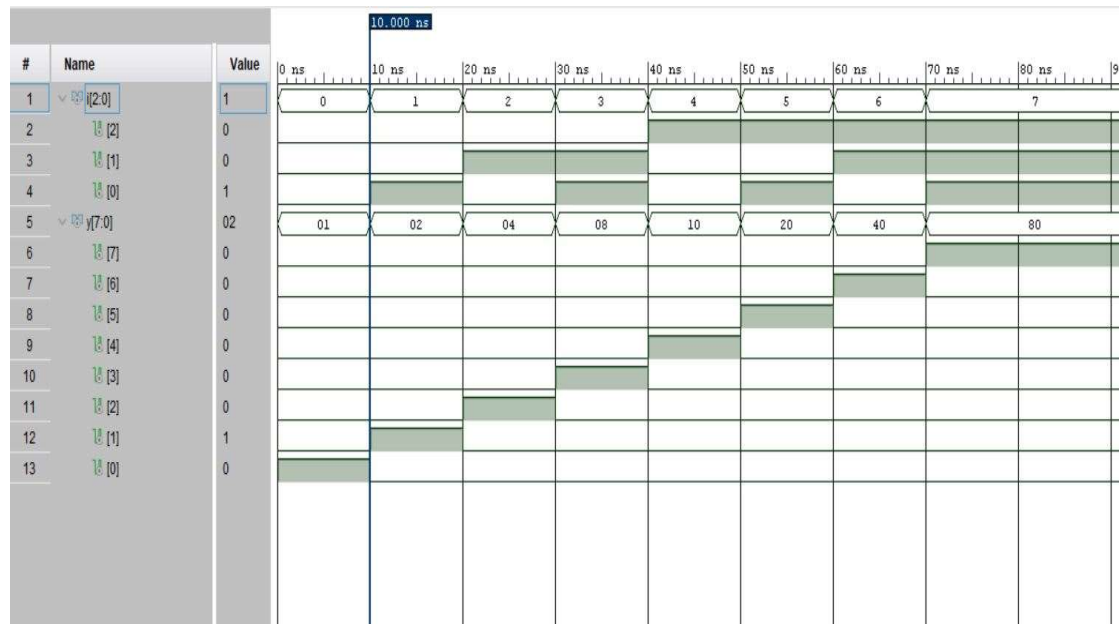

Name	Slack <sup>^</sup> 1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
 Path 1	∞	3	4	8	i[0]	y[1]	5.377	3.778	1.599	∞	input port clock
 Path 2	∞	3	4	8	i[0]	y[3]	5.377	3.778	1.599	∞	input port clock
 Path 3	∞	3	4	8	i[0]	y[5]	5.377	3.778	1.599	∞	input port clock
 Path 4	∞	3	4	8	i[2]	y[7]	5.377	3.778	1.599	∞	input port clock
 Path 5	∞	3	4	8	i[1]	y[0]	5.351	3.752	1.599	∞	input port clock
 Path 6	∞	3	4	8	i[2]	y[2]	5.351	3.752	1.599	∞	input port clock
 Path 7	∞	3	4	8	i[1]	y[4]	5.351	3.752	1.599	∞	input port clock
 Path 8	∞	3	4	8	i[0]	y[6]	5.351	3.752	1.599	∞	input port clock

#### **SYNTHESIS SUMMARY:**

Resource	Utilization	Available	Utilization %
LUT	4	17600	0.02
IO	11	100	11.00

Maximum Combinational Delay: 5.377nSec

**Aim:** Write a VHDL code to implement 8x3 encoder using structural modelling

**Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity Encoder\_8x3 is

Port ( i : in STD\_LOGIC\_VECTOR (7 downto 0);

y : out STD\_LOGIC\_VECTOR (2 downto 0));

end Encoder\_8x3;

architecture Behavioral of Encoder\_8x3 is

component or\_gate

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

y : out STD\_LOGIC);

end component or\_gate;

signal x: std\_logic\_vector(0 to 5);

begin

u1:or\_gate port map(i(4),i(5),x(0));

u2:or\_gate port map(i(6),i(7),x(1));

u3:or\_gate port map(x(0),x(1),y(2));

u5:or\_gate port map(i(2),i(3),x(2));

u6:or\_gate port map(i(6),i(7),x(3));

u7:or\_gate port map(x(2),x(3),y(1));



u8:or\_gate port map(i(1),i(3),x(4));

u9:or\_gate port map(i(5),i(7),x(5));

u10:or\_gate port map(x(4),x(5),y(0));

end Behavioral;

**RTL DIAGRAM:**

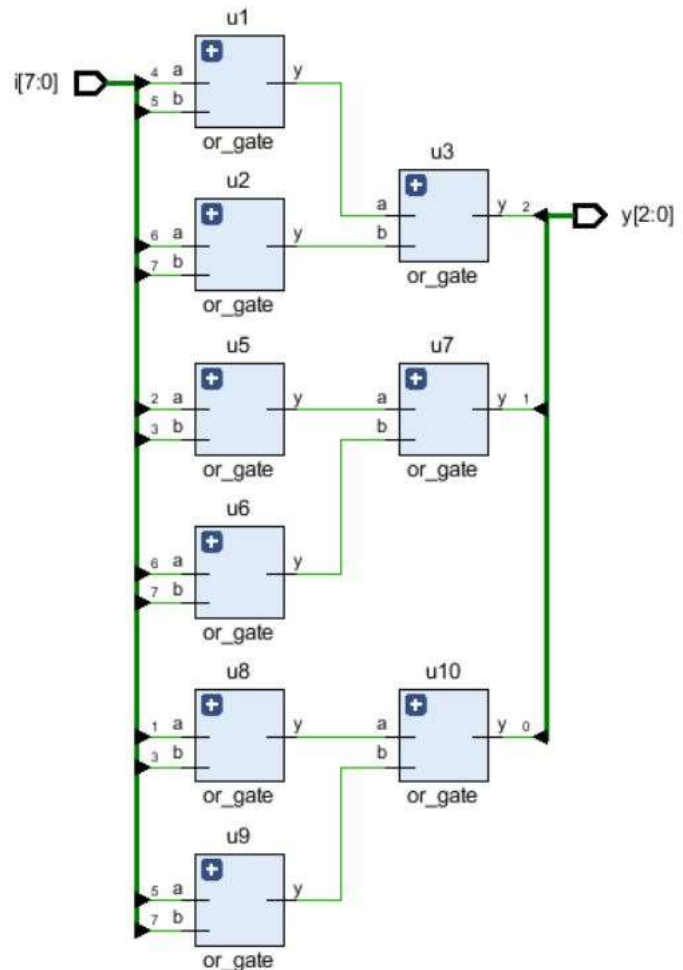 

**Test bench Code :**

```

library IEEE;
use
IEEE.STD_LOGIC_1164.ALL;
entity Tb_Encoder_8x3 is
-- Port ( );
end Tb_Encoder_8x3;

architecture Behavioral of
Tb_Encoder_8x3 is
component Encoder_8x3
is
Port ( i : in
STD_LOGIC_VECTOR (7
downto 0);
y : out
STD_LOGIC_VECTOR (2
downto 0));

```

```

end component
Encoder_8x3;
signal i :
STD_LOGIC_VECTOR (7
downto 0);
signal y :
STD_LOGIC_VECTOR (2
downto 0);
begin
x:Encoder_8x3 port
map(i,y);
process
begin
i<="00000001";
wait for 10ns;
i<="00000010";
wait for 10ns;


```

```

i<="00000100";
wait for 10ns;
i<="00001000";
wait for 10ns;
i<="00010000";
wait for 10ns;
i<="00100000";
wait for 10ns;
i<="01000000";
wait for 10ns;
i<="10000000";
wait;
end process;

end Behavioral;

```

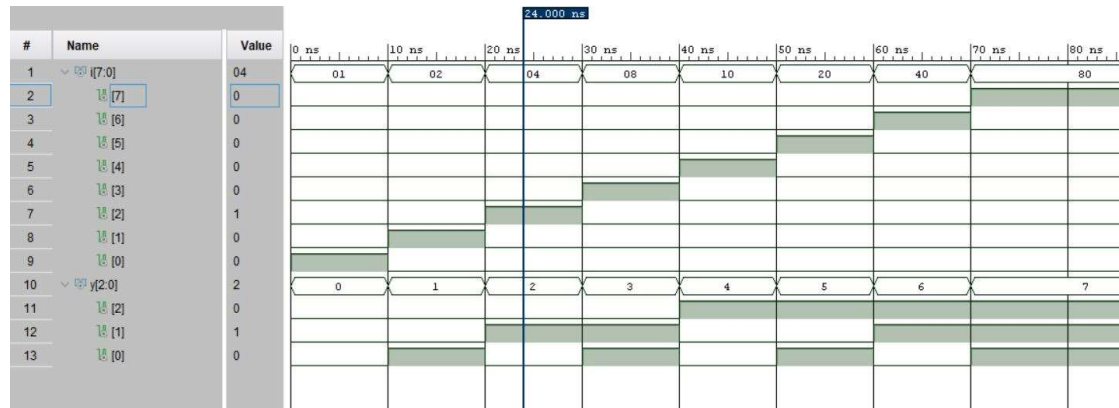**SIMULATION WAVEFORM :**

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	2	i[5]	y[0]	5.351	3.752	1.599	∞	input port clock
Path 2	∞	3	4	2	i[6]	y[1]	5.351	3.752	1.599	∞	input port clock
Path 3	∞	3	4	2	i[6]	y[2]	5.351	3.752	1.599	∞	input port clock

**SYNTHESIS SUMMARY:**

Resource	Utilization	Available	Utilization %
LUT	3	17600	0.02
IO	10	100	10.00

Maximum Combinational Delay: 5.351nSec

**Aim:** Write a VHDL code to implement 1x8 Demultiplexer using behavioral modelling

**Code:**


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Demux1x8 is
Port ( i : in STD_LOGIC;
      y : out STD_LOGIC_VECTOR (0 to 7);
      s : in STD_LOGIC_VECTOR (2 downto 0));
end Demux1x8;

architecture Behavioral of Demux1x8 is

begin
process(i,s)
begin
case(s) is
when "000" => y(0)<=i;
y(1 to 7)<="0000000";
when "001" => y(1)<=i;
y(0)<='0';
y(2 to 7)<="0000000";
when "010" => y(2)<=i;
y(0 to 1)<="00";
y(3 to 7)<="00000";
when "011" => y(3)<=i;
y(0 to 2)<="000";
y(4 to 7)<="0000";
when "100" => y(4)<=i;
y(0 to 3)<="0000";
y(5 to 7)<="000";
when "101" => y(5)<=i;
y(0 to 4)<="00000";
y(6 to 7)<="00";
when "110" => y(6)<=i;
y(0 to 5)<="000000";
y(7)<='0';
when "111" => y(7)<=i;
y(0 to 6)<="0000000";
when others => y<="00000000";
end case;
end process;
end Behavioral;
```

### RTL DIAGRAM:

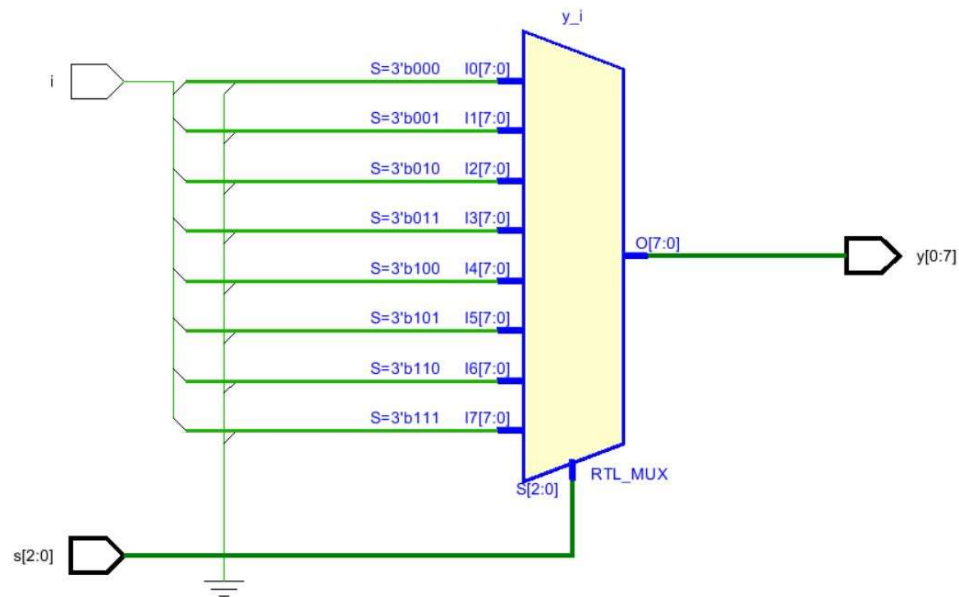

### Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Tb_Demux1x8 is
-- Port ( );
end Tb_Demux1x8;
architecture Behavioral of Tb_Demux1x8 is
component Demux1x8 is
Port ( i : in STD_LOGIC;
y : out STD_LOGIC_VECTOR (0 to 7);
s : in STD_LOGIC_VECTOR (2 downto
0));
end component Demux1x8;
signal i : STD_LOGIC;
signal y : STD_LOGIC_VECTOR (0 to 7);
signal s : STD_LOGIC_VECTOR (2 downto 0);
begin
x1:Demux1x8 port map(i,y,s);
process
begin
i<='0';
s<="000";
wait for 10 ns;
s<="001";
```


```
wait for 10 ns;
s<="010";
wait for 10 ns;
s<="011";
wait for 10 ns;
s<="100";
wait for 10 ns;
s<="101";
wait for 10 ns;
s<="110";
wait for 10 ns;
s<="111";
wait for 50 ns;

i<='1';
s<="000";
wait for 10 ns;
s<="001";
wait for 10 ns;
s<="010";
wait for 10 ns;
s<="011";
wait for 10 ns;
s<="100";
```

```
wait for 10 ns;
s<="101";
wait for 10 ns;
s<="110";
wait for 10 ns;
```

```
s<="111";
wait;
end process;
end Behavioral;
```

### **SIMULATION WAVEFORM :**

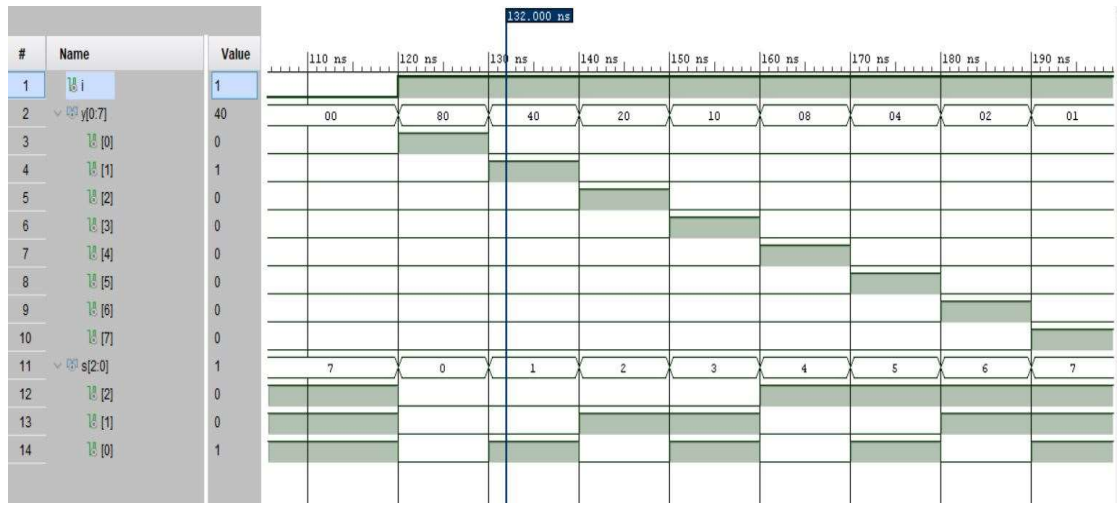

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	8	s[1]	y[0]	5.379	3.780	1.599	∞	input port clock
Path 2	∞	3	4	8	s[0]	y[3]	5.379	3.780	1.599	∞	input port clock
Path 3	∞	3	4	8	s[2]	y[4]	5.379	3.780	1.599	∞	input port clock
Path 4	∞	3	4	8	s[2]	y[7]	5.379	3.780	1.599	∞	input port clock
Path 5	∞	3	4	8	s[2]	y[1]	5.351	3.752	1.599	∞	input port clock
Path 6	∞	3	4	8	s[2]	y[2]	5.351	3.752	1.599	∞	input port clock
Path 7	∞	3	4	8	i	y[5]	5.351	3.752	1.599	∞	input port clock
Path 8	∞	3	4	8	s[1]	y[6]	5.351	3.752	1.599	∞	input port clock

### **SYNTHESIS SUMMARY:**

Resource	Utilization	Available	Utilization %
LUT	4	17600	0.02
IO	12	100	12.00

Maximum Combinational Delay: 5.379nSec



**Aim:** Write a VHDL code to implement 8x1 multiplexer using structural modelling

**Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_8x1 is
    Port ( i : in STD_LOGIC_VECTOR (0 to 7);
          s : in STD_LOGIC_VECTOR (2 downto 0);
          y : out STD_LOGIC);
end Mux_8x1;

architecture Behavioral of Mux_8x1 is
    component or_gate is
        Port ( a : in STD_LOGIC;
              b : in STD_LOGIC;
              y : out STD_LOGIC);
    end component or_gate;

    component and_4input is
        Port ( a1 : in STD_LOGIC;
              a2 : in STD_LOGIC;
              a3 : in STD_LOGIC;
              a4 : in STD_LOGIC;
              y : out STD_LOGIC);
    end component and_4input;
    component not_gate is
        Port ( a : in STD_LOGIC;
              y : out STD_LOGIC);
    end component not_gate;

    signal sb:std_logic_vector(0 to 2);

    signal x:std_logic_vector(0 to 13);
begin
    u0:not_gate port map(s(0),sb(0));
    u1:not_gate port map(s(1),sb(1));
    u2:not_gate port map(s(2),sb(2));

    u3:and_4input port map(sb(0),sb(1),sb(2),i(0),x(0));
    u4:and_4input port map(s(0),sb(1),sb(2),i(1),x(1));
    u5:and_4input port map(sb(0),s(1),sb(2),i(2),x(2));
    u6:and_4input port map(s(0),s(1),sb(2),i(3),x(3));
    u7:and_4input port map(sb(0),sb(1),s(2),i(4),x(4));
    u8:and_4input port map(s(0),sb(1),s(2),i(5),x(5));
    u9:and_4input port map(sb(0),s(1),s(2),i(6),x(6));
    u10:and_4input port map(s(0),s(1),s(2),i(7),x(7));

    u11:or_gate port map(x(0),x(1),x(8));
    u12:or_gate port map(x(2),x(3),x(9));
```


```

u13:or_gate port map(x(4),x(5),x(10));
u14:or_gate port map(x(6),x(7),x(11));
u15:or_gate port map(x(8),x(9),x(12));
u16:or_gate port map(x(10),x(11),x(13));
u17:or_gate port map(x(12),x(13),y);

```

end Behavioral;

### **RTL DIAGRAM:**

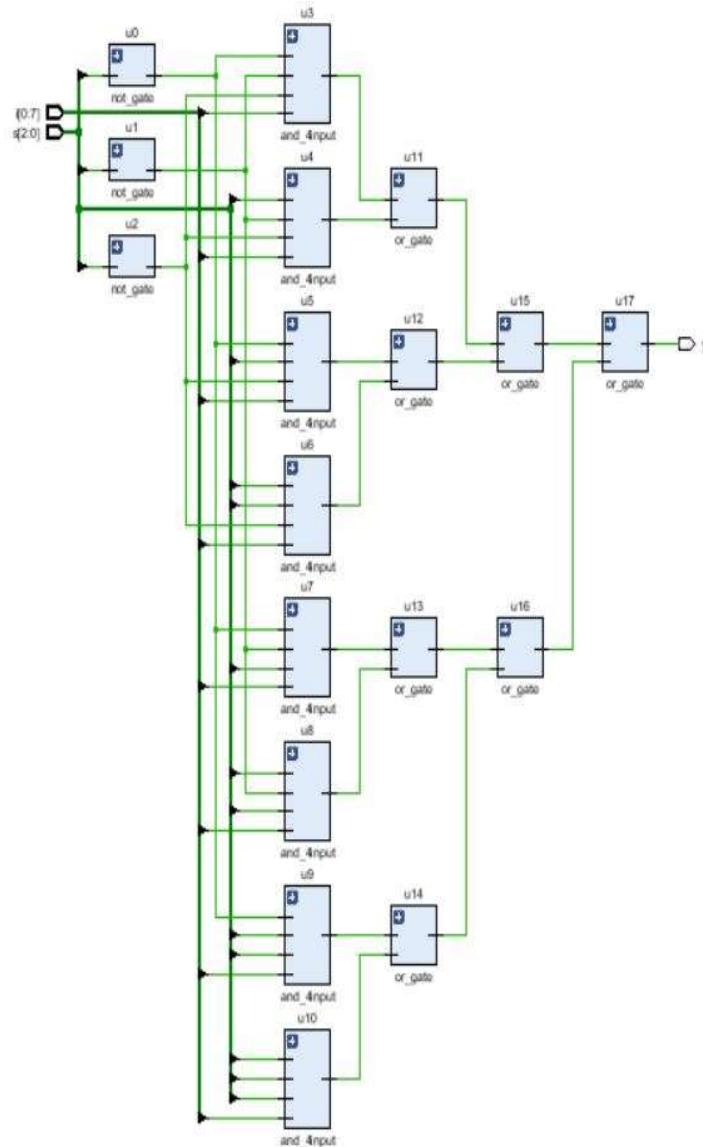

### Test bench Code :

```
library IEEE;
use
IEEE.STD_LOGIC_1164.ALL;
entity Tb_Mux_8x1 is
-- Port ( );
end Tb_Mux_8x1;
architecture Behavioral of
Tb_Mux_8x1 is
component Mux_8x1 is
Port ( i : in
STD_LOGIC_VECTOR (0 to
7);
s : in
STD_LOGIC_VECTOR (2
downto 0);
y : out STD_LOGIC);
end component Mux_8x1;
signal
i1:STD_LOGIC_VECTOR (0
to 7);
signal y: std_logic;
signal s1:
std_logic_vector(2 downto
0);
begin
u1:Mux_8x1 port
map(i1,s1,y);
process
begin
i1<="10000000";
s1<="000";
wait for 10ns;
s1<="001";
wait for 10ns;
s1<="010";
wait for 10ns;
s1<="011";
wait for 10ns;
s1<="100";
wait for 10ns;
s1<="101";
wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait for 50ns;

i1<="00010000";
s1<="000";
wait for 10ns;
s1<="001";
wait for 10ns;
s1<="010";
wait for 10ns;
s1<="011";
wait for 10ns;
s1<="100";
wait for 10ns;
s1<="101";
wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait for 50ns;

i1<="00010000";
s1<="000";
wait for 10ns;

s1<="001";
wait for 10ns;
s1<="010";
wait for 10ns;
s1<="011";
wait for 10ns;
s1<="100";
wait for 10ns;
s1<="101";
wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait for 10ns;
s1<="000";
wait for 10ns;
s1<="001";
wait for 10ns;
s1<="010";
wait for 10ns;
s1<="011";
wait for 10ns;
s1<="100";
wait for 10ns;
s1<="101";
```

```

wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait for 50ns;

i1<="00000010";
s1<="000";
wait for 10ns;
s1<="001";
wait for 10ns;
s1<="010";
wait for 10ns;
s1<="011";
wait for 10ns;


s1<="100";
wait for 10ns;
s1<="101";
wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait for 50ns;

i1<="00000001";
s1<="000";
wait for 10ns;
s1<="001";
wait for 10ns;
s1<="010";

wait for 10ns;
s1<="011";
wait for 10ns;
s1<="100";
wait for 10ns;
s1<="101";
wait for 10ns;
s1<="110";
wait for 10ns;
s1<="111";
wait;
end process;
end Behavioral;

```

### **SIMULATION WAVEFORM :**

 

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	4	5	1	i[4]	y	5.770	4.171	1.599	∞	input port clock

### **SYNTHESIS SUMMARY:**

Resource	Utilization	Available	Utilization %
LUT	2	17600	0.01
IO	12	100	12.00

Maximum Combinational Delay: 5.77nSec