

Practical 8

Aim: Write a VHDL Code to implement 8 bit up down counter using behavioral modeling

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_arith.all;
entity U_D_bh_8B is
    Port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          M : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (7 downto 0)); end if;
end U_D_bh_8B;
```

architecture Behavioral of U_D_bh_8B is

```
begin
process(clk,rst,M)
```


```
    variable t:integer:=0;
    variable t1:STD_LOGIC_VECTOR(7 downto 0);
    begin
    if(rising_edge(clk)) then
```

```
        if(M='1') then
            t:=t + 1;
        elsif(m='0') then
            t:=t - 1;
        end if;
```

```
        t1:= conv_std_logic_vector(t, 8);
```

```
    q<=t1;
    end process;
end Behavioral;
```

RTL DIAGRAM:

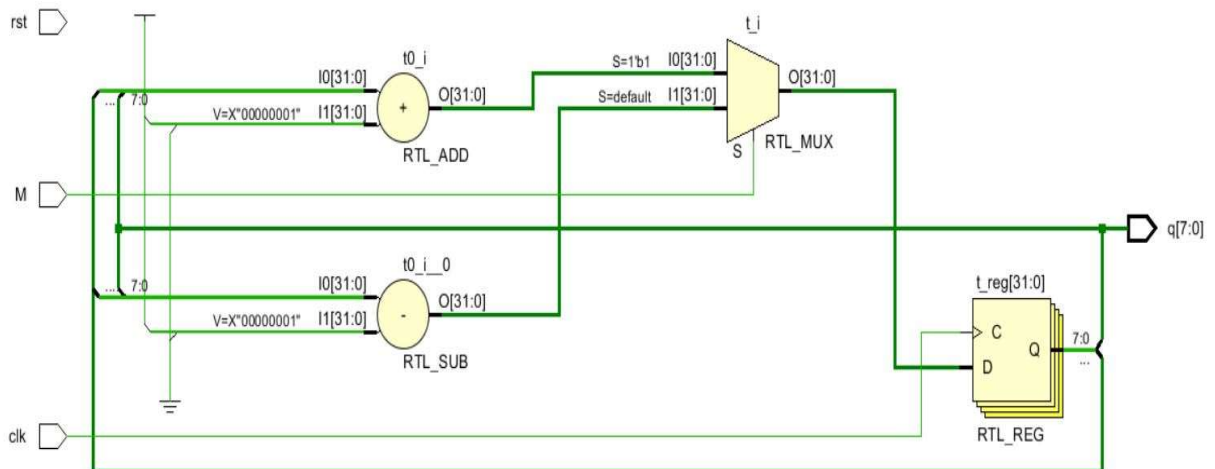

Test bench Code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Tb_U_D_bh_8b is
    -- Port ( );
end Tb_U_D_bh_8b;
```

```
architecture Behavioral of
Tb_U_D_bh_8b is
```

```
    component U_D_bh_8b is
        Port ( clk : in STD_LOGIC;
              rst : in STD_LOGIC;
              M : in STD_LOGIC;
              q : out STD_LOGIC_VECTOR
(7 downto 0));
    end component U_D_bh_8b;
    signal m1,clk1,rst1:std_logic;
```

```
    signal cout1:std_logic_vector(7
downto 0);
```

```
begin
    X1:U_D_bh_8b port
    map(clk1,rst1,m1,cout1);
    process
    begin
```

```

rst1<='0';
wait for 5ns;
rst1<='1';
wait;
end process;

```

```

process
begin
clk1<='0';
wait for 5ns;

```

```

clk1<='1';
wait for 5ns;
end process;

```

```

process
begin
m1<='1';--upcount
wait for 500ns;
m1<='0';--downcount

```


```

wait;
end process;

end Behavioral;


```

SIMULATION WAVEFORM :

 

SYNTHESIS SUMMARY:

Resource	Utilization	Available	Utilization %
LUT	7	17600	0.04
FF	8	35200	0.02
IO	10	100	10.00

 

Name	Slack ^1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	2	t_reg[0]/C	q[0]	4.076	3.276	0.800	∞	
Path 2	∞	2	2	3	t_reg[1]/C	q[1]	4.076	3.276	0.800	∞	
Path 3	∞	2	2	3	t_reg[2]/C	q[2]	4.076	3.276	0.800	∞	
Path 4	∞	2	2	3	t_reg[3]/C	q[3]	4.076	3.276	0.800	∞	
Path 5	∞	2	2	3	t_reg[4]/C	q[4]	4.076	3.276	0.800	∞	
Path 6	∞	2	2	3	t_reg[5]/C	q[5]	4.076	3.276	0.800	∞	
Path 7	∞	2	2	3	t_reg[6]/C	q[6]	4.076	3.276	0.800	∞	
Path 8	∞	2	2	2	t_reg[7]/C	q[7]	4.076	3.276	0.800	∞	
Path 9	∞	4	5	7	M	t_reg[5]/D	2.804	2.004	0.800	∞	input port clock
Path 10	∞	4	5	7	M	t_reg[7]/D	2.785	1.985	0.800	∞	input port clock

Maximum Combinational Delay: 4.076nSec